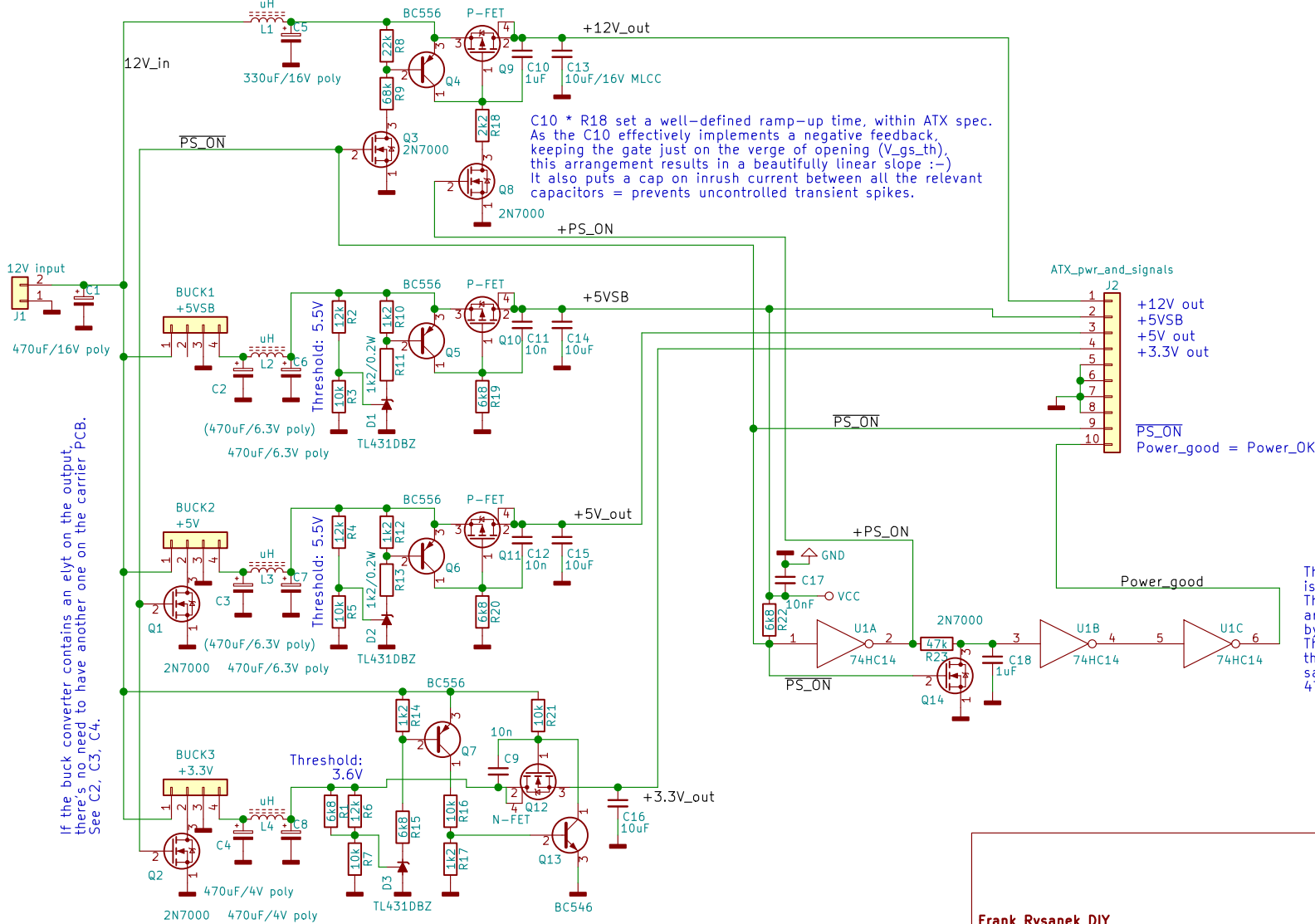


This is an ATX-style multiple buck converter, intended for use in an ATOM-based HTPC, powered by an internal or external 12V mains PSU.

The 12V rail is just filtered and passed through. A power P-FET is used to switch the rail by PS_ON.



C10 * R18 set a well-defined ramp-up time, within ATX spec. As the C10 effectively implements a negative feedback, keeping the gate just on the verge of opening (V_{gs_th}), this arrangement results in a beautifully linear slope :-). It also puts a cap on inrush current between all the relevant capacitors = prevents uncontrolled transient spikes.

If the buck converter contains an electrolytic on the output, there's no need to have another one on the carrier PCB. See C2, C3, C4.

As I don't trust the buck converters very much, I have implemented "over-voltage disconnectors" on the buck-regulated rails. In the 5V rails, both the TL431 and the P-FET can work with that rail voltage. In the 3.3V rail, the TL431's minimum "V_{ce}" doesn't leave much room for the forward voltage of the follow-up PNP BJT's base, and also 3.3V is not enough to fully open a P-FET. Hence the more complex setup, making use of the 12V rail (and an N-FET).

The Power_good output is actually just timer-based. There is no checking if the outputs are really within limits, by the time Power_OK goes high. The fixed time constant is chosen such that all the buck sections should be safely up and running by then. $47k * 1\mu F = cca 50 ms$

Frank Rysanek DIY

Sheet: /
File: atx_3x_buck.sch

Title: ATX triple buck

Size: A4
KiCad E.D.A. kicad 4.0.7

Date:
Rev: 1/1